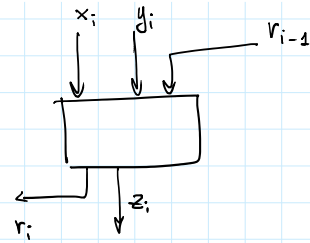


fun "addizionatore di due bit con riporto"



x_i	y_i	r_{i-1}	z_i	r_i
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

expr alg boolean

$$z_i = \bar{x}_i \cdot \bar{y}_i \cdot r_{i-1} + \bar{x}_i \cdot y_i \cdot \bar{r}_{i-1} + x_i \cdot \bar{y}_i \cdot \bar{r}_{i-1} + x_i \cdot y_i \cdot r_{i-1}$$

$$r_i = \bar{x}_i \cdot y_i \cdot r_{i-1} + x_i \cdot \bar{y}_i \cdot r_{i-1} + x_i \cdot y_i \cdot \bar{r}_{i-1} + x_i \cdot y_i \cdot r_{i-1}$$

forma ("canonica")

somma di prodotti


1 della colonna

→ termine: prodotto degli ingressi negati se vengono 0 nella riga
ma negati " = 1 " " "

$$(\bar{x}_i \cdot y_i) \bar{r}_{i-1} + (x_i \cdot \bar{y}_i) r_{i-1} = x_i \cdot y_i \cdot (\bar{r}_{i-1} + r_{i-1}) = x_i \cdot y_i \cdot 1$$


$$r_i = \bar{x}_i \cdot y_i \cdot r_{i-1} + x_i \cdot \bar{y}_i \cdot r_{i-1} + x_i \cdot y_i$$

AND

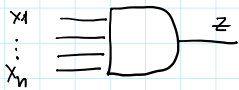


$z = 1$ sse $\forall x_i = 1$

OR

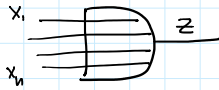

$z = 1$ sse $\exists i x_i = 1$


NOT

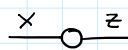

$z = \bar{x}$




$z = \overline{x_1 x_2}$

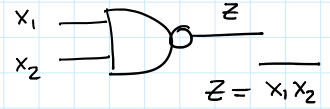


$z = \overline{x_1 x_2}$

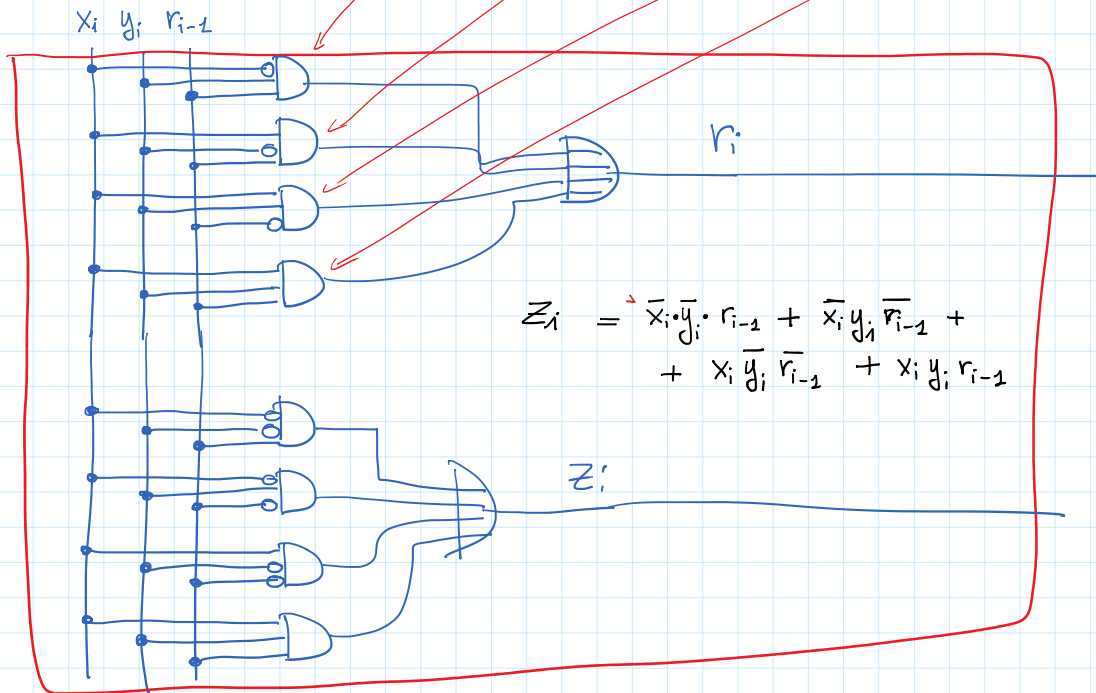$r_i = \bar{x}_i y_i r_{i-1} + x_i \bar{y}_i r_{i-1} + x_i y_i \bar{r}_{i-2} + x_i y_i r_{i-1}$



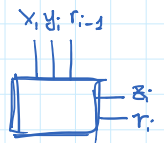$z_i = \bar{x}_i \bar{y}_i r_{i-2} + \bar{x}_i y_i \bar{r}_{i-2} + x_i \bar{y}_i \bar{r}_{i-2} + x_i y_i r_{i-2}$




Porte

max 8 ingressi

introduce un ritardo (tempo)



t_p

AND (16 ingressi)

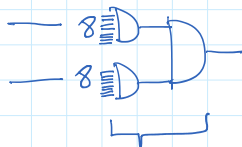

2 livelli di porte $\Rightarrow 2 t_p$

Parità

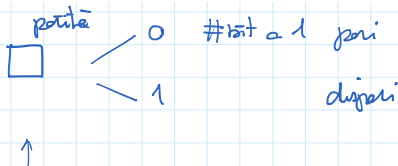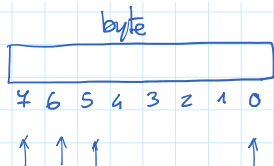


$x_0 \dots$	x_7	Z
0 0 0 0	0 0 0 0	1
0 0 0 0	0 0 0 1	0
0 0 0 0	0 0 1 0	0
0 0 0 0	0 0 1 1	1

$x_0 \bar{x}_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 \bar{x}_6 \bar{x}_7 +$

$128 \cdot 1 \cdot x_0 \bar{x}_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 \bar{x}_6 \bar{x}_7 +$

$\frac{128}{8} = \frac{2^7}{2^3} = 2^4$

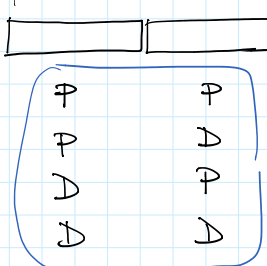


OR 2 "1"

A	A	1
A	A	0
A	A	0
A	A	1

AND 2 ingressi
1 output

$3 = \lceil \lg_8 128 \rceil$

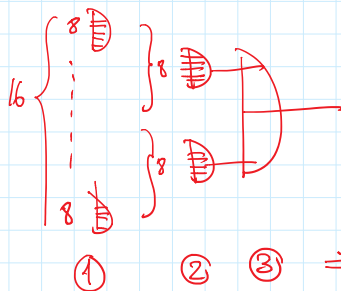

① ② ③ ⇒ 24p


x_1	x_2	x_3	x_4	P
16				8 "1"

p =

1 livello di porte AND (And 4 ingressi)
2 livelli di porte OR (OR da 16 ingressi)

5tp = +


4tp
256

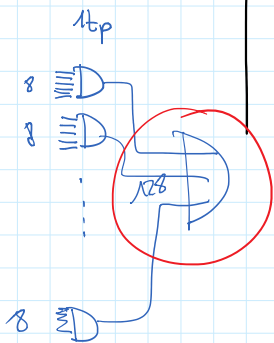

2tp

3tp

Commutatore

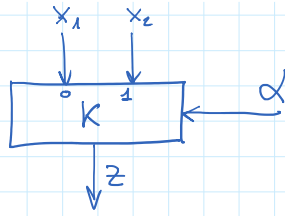


Se $\alpha=0$ then $z = x_1$
 else $z = x_2$

x_1	x_2	α	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



α	x_1	x_2	z
0	1	-	1
0	0	-	0
1	-	0	0
1	-	1	1


$$z = \bar{\alpha}x_1 + \alpha x_2$$


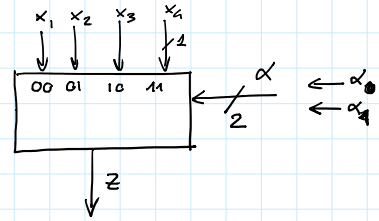


α_0	α_1	x_1	x_2	x_3	x_4	z
0	0	1	-	-	-	1
0	1	-	1	-	-	1
1	0	-	-	1	-	1
1	1	-	-	-	1	1

$$z = \bar{x}_1 \bar{x}_2 \alpha + x_1 \bar{x}_2 \bar{\alpha} + x_1 x_2 \bar{\alpha} + x_1 x_2 \alpha$$
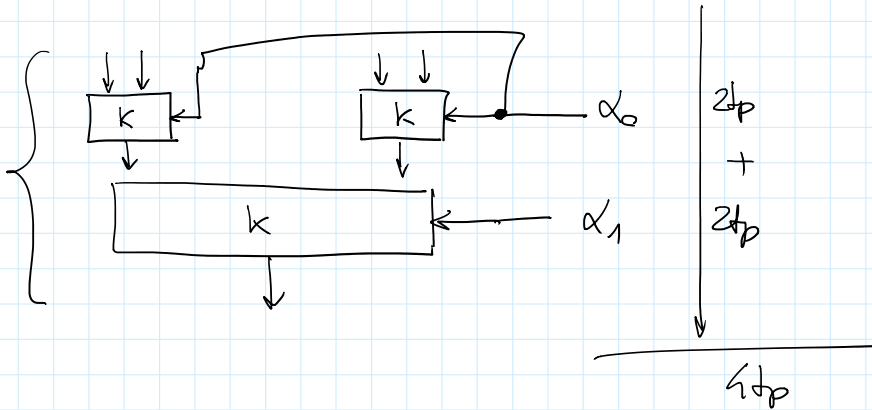
$$z = \bar{\alpha}_0 \bar{\alpha}_1 x_1 + \bar{\alpha}_0 \alpha_1 x_2 + \alpha_0 \bar{\alpha}_1 x_3 + \alpha_0 \alpha_1 x_4$$



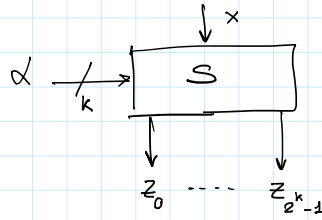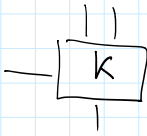

α	x	z_1	z_2
0	1	1	0
1	1	0	1

α_0	α_1	x	z_1	z_2	z_3	z_n
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1
0	0	0	0	0	0	0
0	1	0	0	0	0	0
1	0	0	0	0	0	0
1	1	0	0	0	0	0


selezione

$$z_i = 0 \quad \forall i \neq \alpha$$

$$z_i = x \quad i = \alpha$$


comparatore

x_1	x_2	z
0	0	0
0	1	1
1	0	1
1	1	0

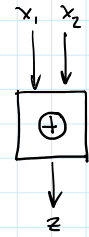

$z = 0$ se $x_1 = x_2$
altrimenti $z = 1$

$$z = x_1 \bar{x}_2 + \bar{x}_1 x_2$$

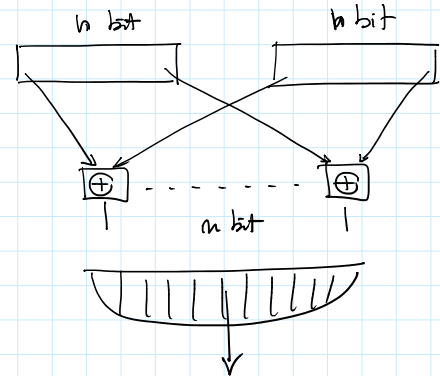

7

mercoledì 21 settembre 2016 13:59

17

mercoledì 21 settembre 2016 13:59

